

## Carry Look-Ahead Adder

The carry look-ahead adder is based on computing the carry bits  $C_i$  prior to the summation. The carry look-ahead logic makes use of the relationship between the carry bits  $C_i$  and the input bits  $A_i$  and  $B_i$ . We define two variables  $G_i$  and  $P_i$ , named as the generate and the propagate functions, as follows:

$$\begin{aligned} G_i &= A_i B_i , \\ P_i &= A_i + B_i . \end{aligned}$$

Then, we expand  $C_1$  in terms of  $G_0$  and  $P_0$ , and the input carry  $C_0$  as

$$C_1 = A_0 B_0 + C_0(A_0 + B_0) = G_0 + C_0 P_0 .$$

Similarly,  $C_2$  is expanded in terms  $G_1$ ,  $P_1$ , and  $C_1$  as

$$C_2 = G_1 + C_1 P_1 .$$

When we substitute  $C_1$  in the above equation with the value of  $C_1$  in the preceding equation, we obtain  $C_2$  in terms  $G_0$ ,  $G_1$ ,  $P_0$ ,  $P_1$ , and  $C_0$  as

$$C_2 = G_1 + C_1 P_1 = G_1 + (G_0 + C_0 P_0) P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1 .$$


Proceeding in this fashion, we can obtain  $C_i$  as function of  $C_0$  and  $G_0, G_1, \dots, G_i$  and  $P_0, P_1, \dots, P_i$ . The carry functions up to  $C_4$  are given below:

$$\begin{aligned} C_1 &= G_0 + C_0 P_0 , \\ C_2 &= G_1 + G_0 P_1 + C_0 P_0 P_1 , \\ C_3 &= G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2 , \\ C_4 &= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3 . \end{aligned}$$

The carry look-ahead logic uses these functions in order to compute all  $C_i$ s in advance, and then feeds these values to an array of EXOR gates to compute the sum vector  $S$ . The  $i$ th element of the sum vector is computed using

$$S_i = A_i \oplus B_i \oplus C_i .$$

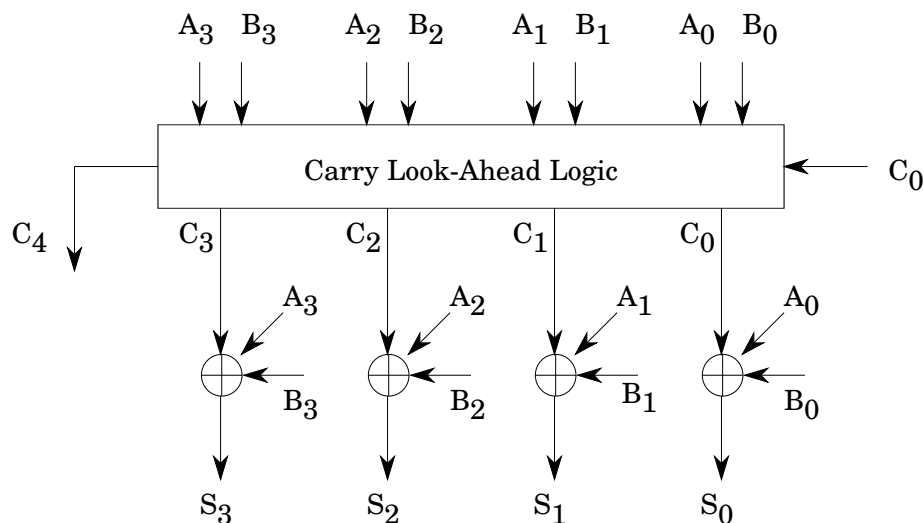The carry look-ahead adder for  $k = 3$  is illustrated below.



The CLA does not scale up very easily. In order to deal with large operands, we have basically two approaches:

- The block carry look-ahead adder: First we build small (4-bit or 8-bit) carry look-ahead logic cells with section generate and propagate functions, and then stack these to build larger carry look-ahead adders [2, 7, 3].
- The complete carry look-ahead adder: We build a complete carry look-ahead logic for the given operand size. In order to accomplish this task, the carry look-ahead functions are formulated in a way to allow the use of the parallel prefix circuits [1, 4, 5].

The total delay of the carry look-ahead adder is  $O(\log k)$  which can be significantly less than the carry propagate adder. There is a penalty paid for this gain: The area increases. The block carry look-ahead adders require  $O(k \log k)$  area, while the complete carry look-ahead adders require  $O(k)$  area by making use of efficient parallel prefix circuits [5, 6]. It seems that a carry look-ahead adder larger than 256 bits is not cost effective, considering the fact there are better alternatives, e.g., the carry save adders. Even by employing block carry look-ahead approaches, a carry look-ahead adder with 1024 bits seems not feasible or cost effective.

## References

- [1] R. P. Brent and H. T. Kung. A regular layout for parallel adders. *IEEE Transactions on Computers*, 31(3):260–264, March 1982.
- [2] K. Hwang. *Computer Arithmetic, Principles, Architecture, and Design*. John Wiley & Sons, 1979.

- [3] I. Koren. *Computer Arithmetic Algorithms*. Prentice-Hall, 1993.
- [4] D. C. Kozen. *The Design and Analysis of Algorithms*. Springer, 1992.
- [5] R. Ladner and M. Fischer. Parallel prefix computation. *Journal of the ACM*, 27(4):831–838, October 1980.
- [6] S. Lakshmiarahan and S. K. Dhall. *Parallelism in the Prefix Problem*. Oxford University Press, 1994. In press.
- [7] S. Waser and M. J. Flynn. *Introduction to Arithmetic for Digital System Designers*. Holt, Rinehart and Winston, 1982.